
UM-SJTU JOINT INSTITUTE

PHYSICS LABORATORY
(Vp241)

LABORATORY REPORT

EXERCISE 5

RC, RL, AND RLC CIRCUIT

Name: Zhiyuan Ning ID:522370910079 Group:17
Date: November 11, 2023

[rev4.1]

1 Introduction

The objective of the experiment is to investigate the phenomenon of the dynamic processes in RC, RL, and RLC series circuits and meanwhile examine the relationship between features ranging from half-life period to resonant behavior based on the measured data.

The model of the experiment mainly consists of three parts: RC, RL, and RLC series circuits (stable and resonant), including exponential function and damping oscillation.

Firstly, for RC series circuits: for the process of charging:

$$RC\dot{U}_C + U_C = \epsilon \quad (1)$$

whose solution is:

$$U_C = \epsilon(1 - e^{-\frac{t}{RC}}) \quad (2)$$

and for the process of discharging:

$$RC\dot{U}_C + U_C = 0 \quad (3)$$

$$U_C = \epsilon e^{-\frac{t}{RC}} \quad (4)$$

So the volt of the resistor R U_R is respectively:

$$U_R = \pm \epsilon e^{-\frac{t}{RC}} \quad (5)$$

Secondly, similarly for RL series circuits:

$$L\dot{I} + IR = \epsilon \quad (6)$$

$$I = \frac{\epsilon}{R}(1 - e^{-\frac{Rt}{L}}) \quad (7)$$

$$L\dot{I} + IR = 0 \quad (8)$$

$$I = -\frac{\epsilon}{R}e^{-\frac{Rt}{L}} \quad (9)$$

So the volt of the resistor R, U_R is respectively:

$$U_R = IR = \pm \epsilon e^{-\frac{Rt}{L}} \quad (10)$$

Thirdly, for RCL series circuits: when connected with square waves:

$$LC\ddot{U}_C + RC\dot{U}_C + U_C = \epsilon \quad (11)$$

let $\beta = \frac{R}{2L}$, $\omega_0 = \frac{1}{\sqrt{LC}}$, $\omega = \sqrt{|\omega^2 - \beta^2|}$ then taking the initial value, solution is:

$$U_C = \begin{cases} \epsilon(1 - e^{-\beta t}(\cos\omega t + \frac{\beta}{\omega}\sin\omega t)) & , \omega^2 - \beta^2 < 0 \\ \epsilon(1 - (1 + \beta t)e^{-\beta t}) & , \omega^2 - \beta^2 = 0 \\ \epsilon(1 - \frac{1}{2\omega}e^{-\beta t}[(\beta + \omega)e^{\omega t} - (\beta - \omega)e^{-\omega t}]) & , \omega^2 - \beta^2 > 0 \end{cases} \quad (12)$$

when connected with sinuous waves:

$$LC\ddot{U}_C + RC\dot{U}_C + U_C = u \cos \omega_d t \quad (13)$$

As forced oscillation, the resonant frequency is:

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (14)$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad (15)$$

And the phase difference between the current and the voltage in the circuit is :

$$\phi = \arctan\left(\frac{\omega_d L - \frac{1}{\omega_d C}}{R}\right) \quad (16)$$

The quality factor of the resonant circuit is:

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} \quad (17)$$

2 Experimental setup

According to the lab manual, the general equipment of the experiment mainly consists of a signal generator, an oscilloscope, a digital meter, a wiring board and the circuit elements(resistors, capacitors and inductors)

The Oscilloscope used in the experiment is comparatively old, and the reading is slightly varying in time, so the measurement of the half-life period and U_R might not be accurate.

3 Measurements

3.1 Stable session(RC, RL, and RLC)

The half-life period and the parameters of the elements(resistance, capacitance and inductance) are measured and the obtained data for RC, RL, and RLC series circuits is presented in Table1, Table 2, and Table3 respectively.

$R99.65[\Omega] \pm 0.005[\Omega]$	$f1000.000[Hz] \pm 0.001[Hz]$	$\epsilon4.16[V] \pm 0.08[V]$
$C0.454[\mu F] \pm 0.0005[\mu F]$	$T_{1/2}36[\mu s] \pm 2[\mu s]$	

Table 1: Data for the measurement of RC series circuit.

$R99.65[\Omega] \pm 0.005[\Omega]$	$f1000.000[Hz] \pm 0.001[Hz]$	$\epsilon4.16[V] \pm 0.08[V]$
$L0.01[H] \pm 0[H]$	$T_{1/2}72[\mu s] \pm 2[\mu s]$	

Table 2: Data for the measurement of RL series circuit.

$L0.01[H] \pm 0[H]$	$C99.8[nF] \pm 0.05[nF]$	$\epsilon4.16[V] \pm 0.08[V]$
$f1000.000[Hz] \pm 0.001[Hz]$	$\beta t = 1.68$	$T_{1/2}70[\mu s] \pm 2[\mu s]$

Table 3: Data for the measurement of the critically damped RLC series circuit.

3.2 Resonant RLC series circuit

Then U_R w.r.t different driving frequency(the frequency of the input sinuous wave). The obtained data is presented in Table 4 .

4 Results

The results of the experiment is calculated as follows:

4.1 Stable session(RC, RL, and RLC)

From the introduction, we can know that the theoretical value of the half-life period of the charging process of the RC series circuit is:

$$T_{1/2} = RC \ln 2 \approx 31.35874\mu s$$

which is close to (still a bit smaller than) the experimental value. The picture is:

□f1.jpg

Figure 1: the picture of the RC

From the introduction, we can know that the theoretical value of the half-life period of the charging process of the RL series circuit is:

$$T_{1/2} = \frac{L}{R} \ln 2 \approx 69.95582\mu s$$

	$R99.65[\Omega] \pm 0.005[\Omega]$	$L0.01[H] \pm 0[H]$	$C0.454[\mu F] \pm 0.0005[\mu F]$
		$f_02.3621[kHz] \pm 0.1[Hz]$	$\epsilon4.16[V] \pm 0.08[V]$
		$U_R[V] \pm 0.08[V]$	$f[Hz] \pm 0.001[Hz]$
1		2.16	1.400000
2		2.4	1.500000
3		2.64	1.600000
4		2.88	1.700000
5		3.12	1.800000
6		3.36	1.900000
7		3.52	2.000000
8		3.68	2.100000
9		3.76	2.200000
10		3.84	2.300000
11		3.84	2.400000
12		3.76	2.500000
13		3.68	2.600000
14		3.6	2.700000
15		3.44	2.800000
16		3.36	2.900000
17		3.12	3.000000
18		3.04	3.100000
19		2.96	3.200000
20		2.8	3.300000
21		2.64	3.400000

Table 4: Data for the measurement of the U_R vs. f dependence for RLC resonant circuit.

□f2.jpg

Figure 2: the picture of the RL

which is close to (still a bit smaller than) the experimental value. The picture is:

From the introduction, we can know that the theoretical value of the half-life period of the charging process of the critical damped RLC series circuit is got by solving $(1 + \beta t)e^{-\beta t} = 1/2$:

$$T_{1/2} \approx 63.20583\mu s$$

which is close to (still a bit smaller than) the experimental value (and will be discussed in the discussion section). The picture of three damping cases is:

□f3.jpg

Figure 3: the picture of the underdamped RCL

□f4.jpg

Figure 4: the picture of the critically damped RCL

□f5.jpg

Figure 5: the picture of the overdamped RCL

4.2 Resonant RLC series circuit

As is stated in the introduction part, the resonant frequency is calculated to be:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \approx 2.3621kHz$$

The current I can be calculated with $I = U_R/R$. The phase difference can be calculated with $\phi = \arctan(\frac{\omega_d L - \frac{1}{\omega_d C}}{R})$. Then the relationship between f and I is shown in the graphs below:

f6.png

Figure 6: the graph of I/I_m vs. f/f_0

f7.png

Figure 7: the graph of ϕ vs. f/f_0

The Quality factor can be calculated with:

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} \approx 1.489364 \times 10^{-3}$$

5 Conclusions and discussion

This experiment provide insight into the features of RC, RL, and RLC series circuits (half-life period, driven and damped oscillation, phase difference,

resonant frequency and quality factor). In addition of learning the pattern and properties of the voltage changes in different circuits, the experiment also shows how the phase difference and amplitude varies with respect to the frequency of the sinuous wave.

The fundamental source of inaccuracy of the method adopted is that while moving the cursors, I may have forgotten to keep the X1 fixed when moving X2 because of the different operation logic of different oscilloscope. So the overall measurement of the half-life period is bigger than expected.

The precision of the measurements, can be further increased by adopting other method that measures the phase difference by machine to further examine the results deducted from calculation. Also, choosing more stable and percise oscilloscope helps.

In real life, these circuits can be used in multiple aspects like Tuned circuits, Power factor correction, and signal processing

A Datasheet

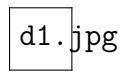


Figure 8:

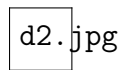


Figure 9: